

Experiment - 1


Objective - Energy band gap of semiconductors by reverse saturation current method.

Apparatus used - One variable DC Regulated Power supply. Two meters to measure voltage, reverse saturation current, temperature.

Open, PN Junction diode, Junction wire, Generalised electric oven, measuring thermometer electric.

Theory - At times in the case of insulators, the region between highest occupied band (valence band) and very wide. This is energy gap. This is identified by Eg and is about 3 to 7 eV (electron volt) in case of insulators, this energy gap is quite small for example in case of germanium $E_g = 0.7 \text{ eV}$ and in case of silicon $E_g = 1.17 \text{ eV}$.

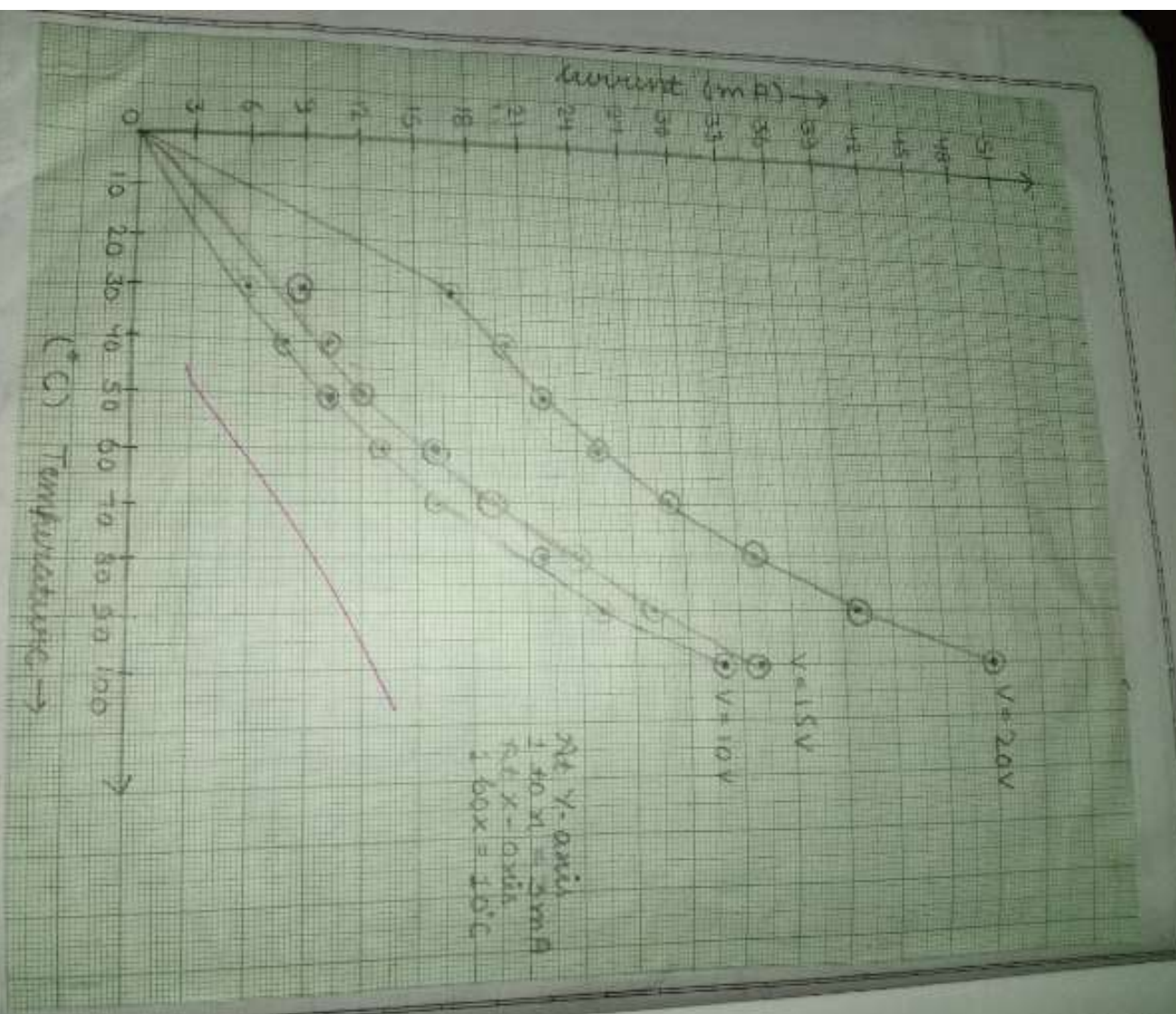In semi-conductors at low temperatures, there are few changes to make so conductivity is quite low. At higher temperatures the electron can absorb levels from into action and finally semiconductors can force the conductivity high. In addition to



Expt. No.


The dependence of the electrical conductivity on the number of free charges, it also depends on their mobility. However mobility of the charge carriers some what decrease with the increasing temperature.

Observation Table -

S.No	Temperature	Current (mA)		
		V=10V	V=15V	V=20V
1.	30°C	6	9	17
2.	40°C	8	10	20
3.	50°C	10	12	22
4.	60°C	13	17	25
5.	70°C	16	19	29
6.	80°C	22	24	34
7.	90°C	25	28	40
8.	100°C	32	34	48

Result - Graph between Reverse saturation current and temperature for energy band gaps

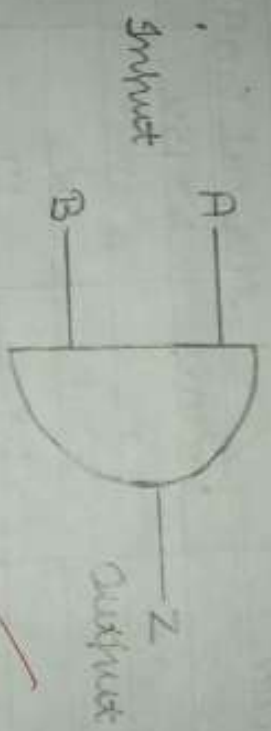Teacher's Signature: *[Signature]*
 10/10/25



AND gate



Expt. No. _____

Experiment - 2

Object - Study and verification of AND gate using TTL IC-7408

Apparatus used - Bread board, connecting leads, LED's, IC 7408.

Theory - The AND gate performs logical multiplication. AND gate circuit has two inputs and one output. Whenever both the inputs are high or 1 the output for this will be logic high or 1 and low otherwise. The truth table for AND gate is;

Inputs		Output
A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1

Result - The operation of logic gate is successfully verified.

Teacher's Signature.....

[Signature]
16/02/26



OR gate

Experiment - 3

Object - Study and verification of OR gate using TTL IC 7432

Apparatus used - Bread board, connecting leads, LED's, TC 7432.



Theory - The OR gate performs logical addition OR gate circuit has two inputs and one output whenever both the inputs are low or 0 or one output for this will be logic low or 0 and high or 1 otherwise. The truth table for OR gate is

Inputs	Output
A B	Z
0 0	0
0 1	1
1 0	1
1 1	1

Result - The operation of logic gate is successfully verified.

Teacher's Signature

[Signature]
16/10/21/26

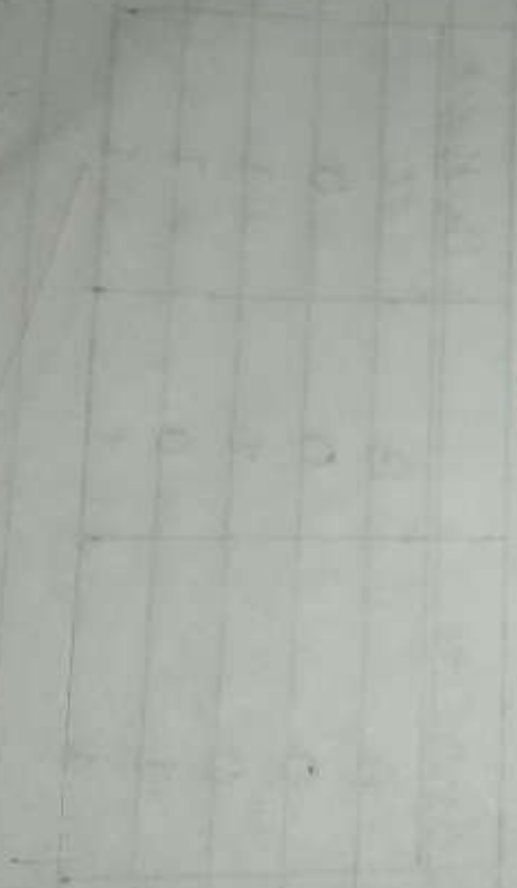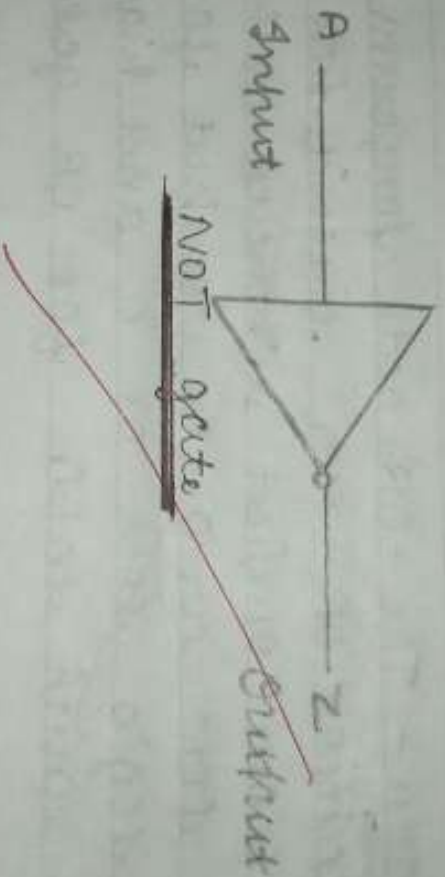

Experiment - 4

Object - Study and verification of NOT gate using TTL IC 7404.

Apparatus used - Bread board, connecting leads, LED's, IC 7404.

Theory - The inverter (NOT circuit) perform a basic logic function called inversion or complementation. This gate has only one input and one output. NOT gate is called the inverter, because output state is always opposite to the input state. When the input is low or 0, the output is logic high or 1 and vice versa.

Input	Output
0	1
1	0

Result - The operation of logic gate is successfully verified.



~~NAND gate~~

Input A	Input B	Output C
0	0	1
0	1	1
1	0	1
1	1	0

Expt. No. _____

Experiment - 5

Object - Study and verification of NAND gate and use as universal gate using TTL IC 7400.

Apparatus used - Bread board, connecting leads, LED's, IC 7400.

Theory - The term NAND is a contraction of NOT-AND and implies an AND function with complemented output. NAND gate has two inputs and one output. Whenever at least one of the inputs is low, the output voltage will be high. If both inputs are high, then the output logic is low. The truth table for NAND gate is

Input		Output
A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

Result - The operation of logic gate is successfully verified.

Teacher's Signature

Ravi
17/02/26



NOR gate

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

Expt. No. _____

Experiment - 6

Object - Study and verification of NOR gate and use as universal gate using TTL IC 7402.

Apparatus used - Bread board, connecting leads, LED's IC 7402.

Theory - The term NOR is a contraction of NOT-OR and implies an OR function with an inverted output. The circuit has two inputs and one output. Whenever at least one of the input is high or 1, the output will be low or 0. If both inputs are low, then output is high or 1. The truth table for NOR gate is

Input		Output
A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

Result - The operation of logic gate is successfully verified.

Teacher's Signature

Ravi
17/02/26



XOR gate

Expt. No. _____

Experiment - 7

Object - Study and verification of EX-OR gate using TTL IC 7486.

Apparatus used - Bread board, connecting leads, LED's IC 7486.


Theory - EX-OR gate circuit has two inputs and one output. Whenever both the inputs are the same, the corresponding output will be low otherwise the output will be logic high or 1. The truth table for EX-OR gate is;

Input		Output
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0


Result - The operation of logic gate is successfully verified.

Teacher's Signature

Ravi
17/02/26

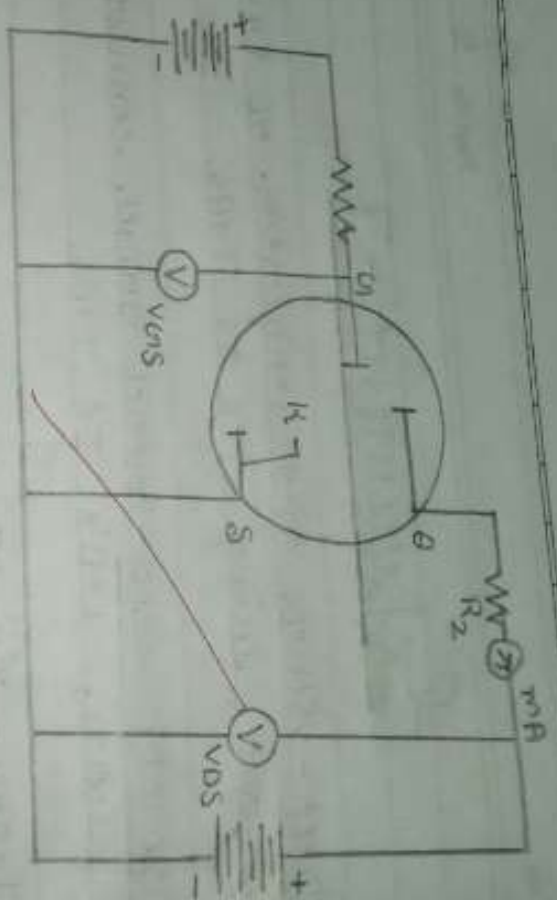

Graph:-

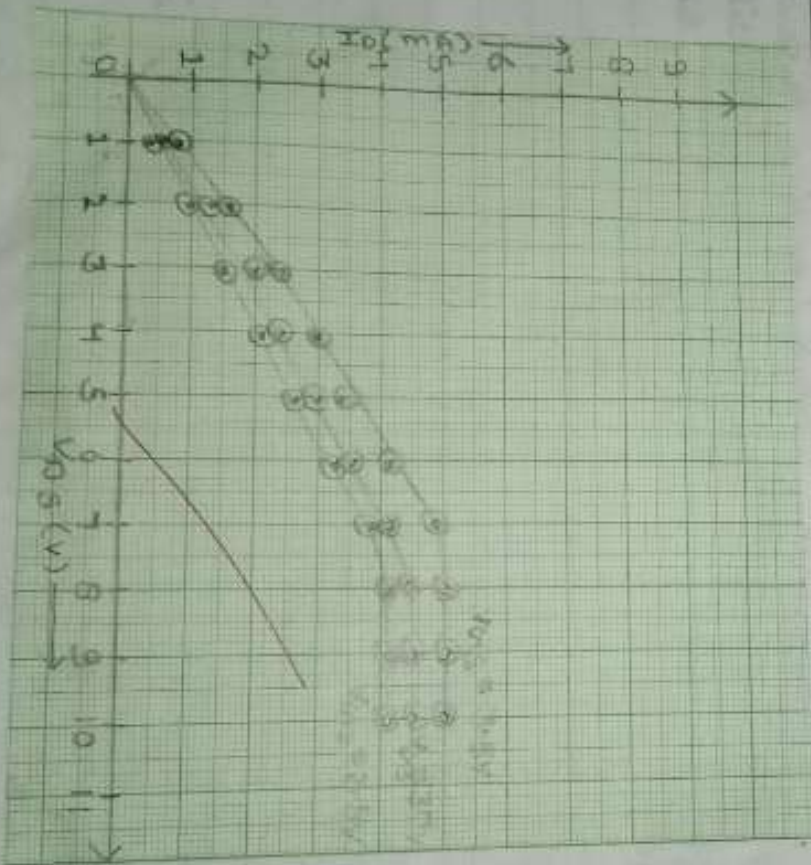

Experiment - 8

Objective - To study the characteristics of MOSFET.


Apparatus used - MOSFET, resistors, connecting wires, ammeter, voltmeter, dc power supply etc.

Theory - A MOSFET (Metal-oxide semiconductor field-effect transistor) is a voltage-controlled three terminal device (source, drain and gate) that uses an electric field generated by the gate voltage to modulate the conductivity between the source and drain, controlling current flow. N-channel MOSFET, P-channel MOSFET, enhancement mode, depletion mode.

Observation - a) Output (drain) characteristics

V_{GS} (Volts)	$V_{DS} = 3.5V$ I_D (mA)	$V_{DS} = 3.7V$ I_D (mA)	$V_{DS} = 3.8V$ I_D (mA)
0	0	0	0
1	0.5	0.6	0.4
2	1.3	1.5	0.9
3	1.9	2.3	1.6
4	2.4	2.9	2.4

Synopsis -

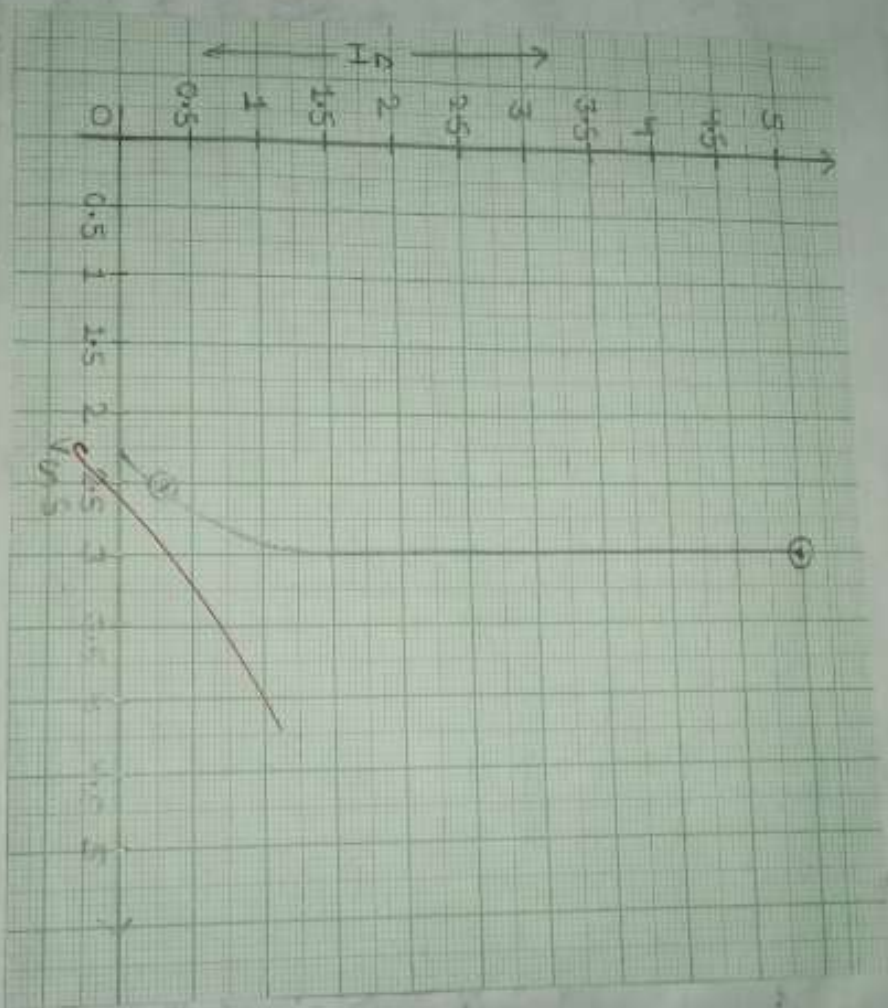

Expt No. _____

5	3	3.3	2.9
6	3.5	4.1	3.5
7	4.2	4.7	4.3
8	4.5	5	4.7
9	5	5	5
10	5	5	5

(f) Transfer characteristics

		$V_{DS} = 20V$	
		V_{GS}	I_{DS}
1	0	0	0
2	0.5	0	0
3	1	0	0
4	1.5	0	0
5	2	0	0
6	2.5	0.3	
7	3	5	


Result - The characteristics of MOSFET has been plotted.

Precaution - (1) All the wire connections should be proper.

- The device should be handled carefully.
- They should never be connected or disconnect when the power is ON.

Teacher's Signature

P. P. P.
24/09/26

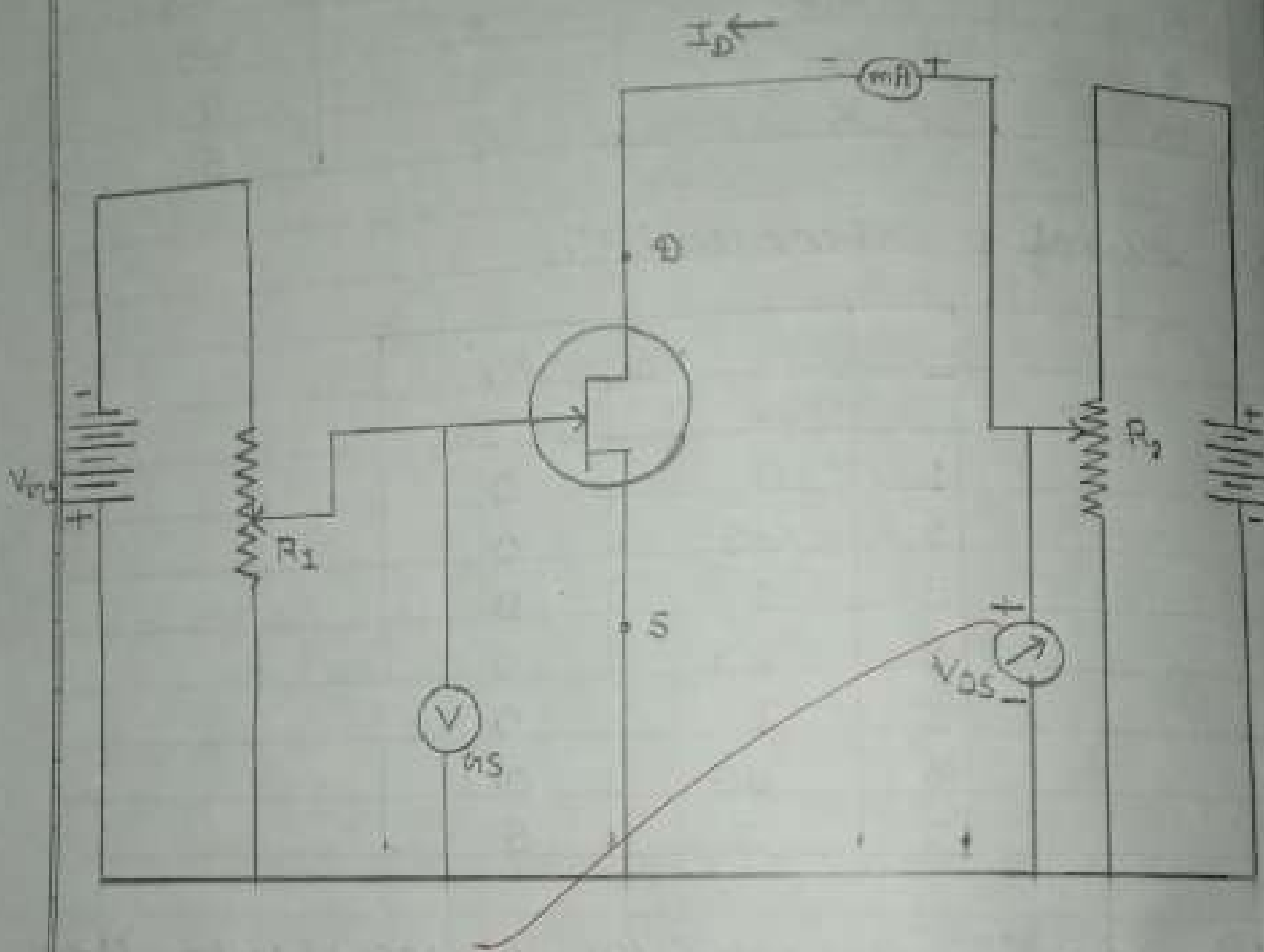

Expt. No.

Experiment - 9

Object - To plot the V-I characteristics of FET at different gate voltages.

Apparatus used - FET apparatus, connection wires.

Theory - The field effect Transistor or Junction field effect Transistor is fabricated by using monolithic Silicon technology. This device comprises of high input resistance as compared to bipolar transistors. FET's are mainly of two types.

- (1) Junction field effect Transistor (JFET).
- (2) Metal-Oxide Semiconductor field effect Transistor (MOSFET).


Observation Table → (A)

SR No.	V _{GS} (Volts)	I _D (mA) FOR		
		V _{DS} = 0V	V _{DS} = 0.25V	V _{DS} = 0.5V
0	0	0	0	0
1	2.5	2.5	1.75	0
2	5	5	2.75	0.25
3	7.5	6.75	3.25	0.50


Teacher's Signature.....

Graph -

(A)

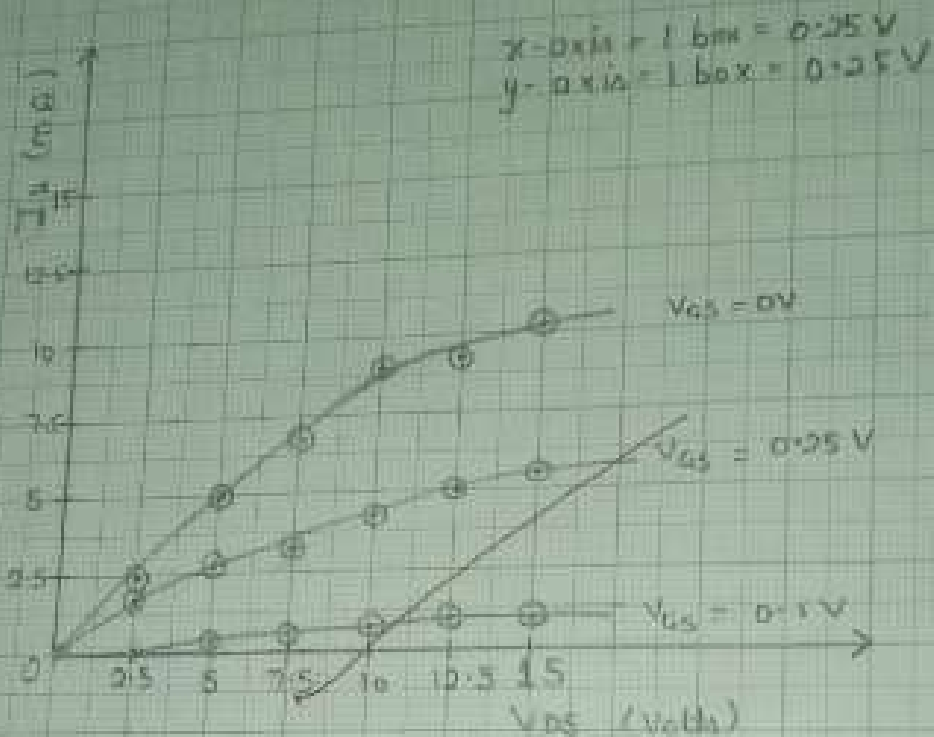

(B) Graph -

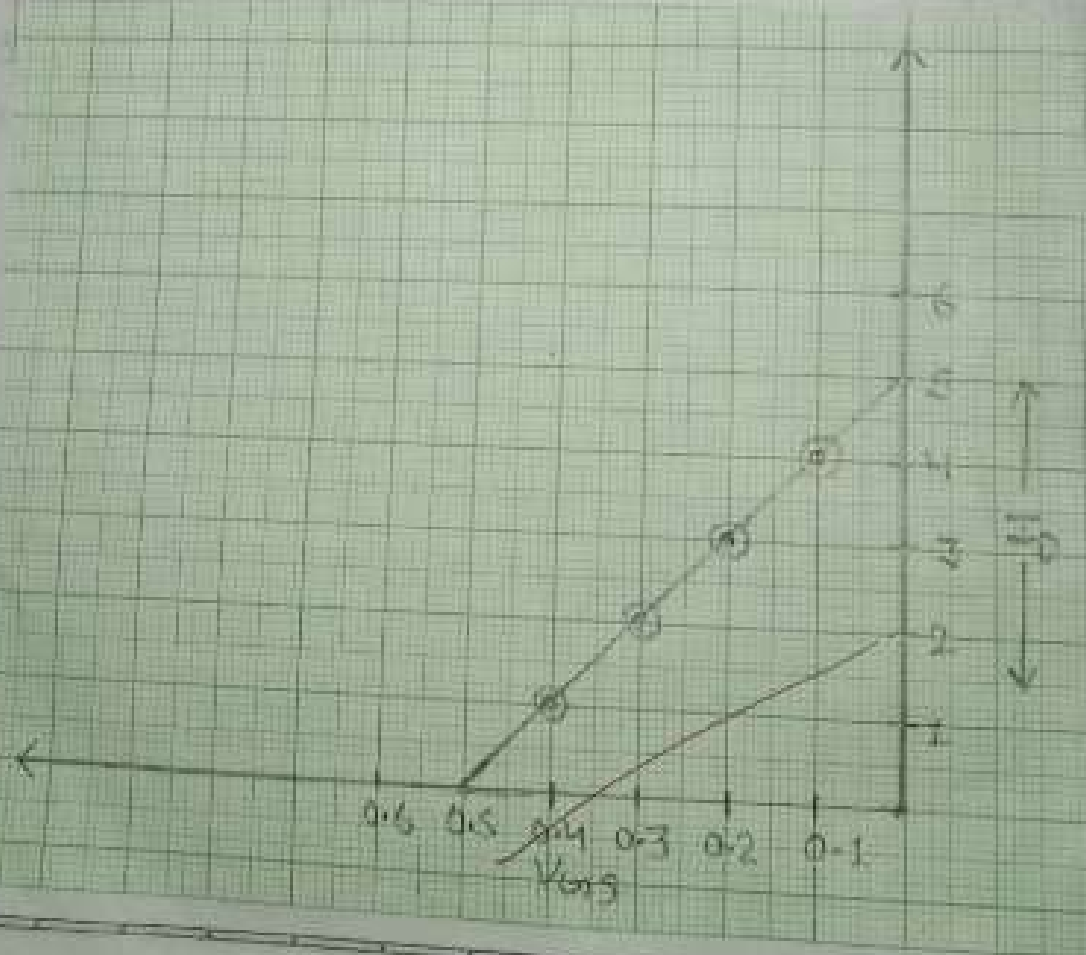

Page No.

4	10	8.25	4.25	0.75
5	12.5	9.25	5	1.00
6	15	10.25	5.50	1.00

(8)

S. No.	For constant $V_{GS} = 5V$	
	V_{DS} (Volts)	I_D (mA)
1	0	5
2	0.1	4.25
3	0.2	3.25
4	0.3	2.00
5	0.4	1.00
6	0.5	0

Result - The characteristics of F.E.T has been plotted graph.

Precaution - All the wire connections should be proper.

(2) The device should be handled carefully.

(3) These should never be connected or disconnect when the power is ON.

Expt. No.

Experiment - 10

Object - Study of characteristics of UJT.


Apparatus Required - Power supply, UJT, characteristic, connecting leads, Ammeter, Voltmeter.

- Theory - A uni junction transistor is a three terminal semiconductor device having two doped regions. In the three terminals, it has one emitter (E) & two Bases (B_1 & B_2). It has only one junction. It consist of an n-type silicon bar which is lightly doped. Two end connections are taken from the base called B_1 & B_2 . A heavily doped P-region is diffused to n-bar nearer to B_2 .

Observation Table -

$$V_{B_2B_1} = 10 \text{ V}$$

Synch-

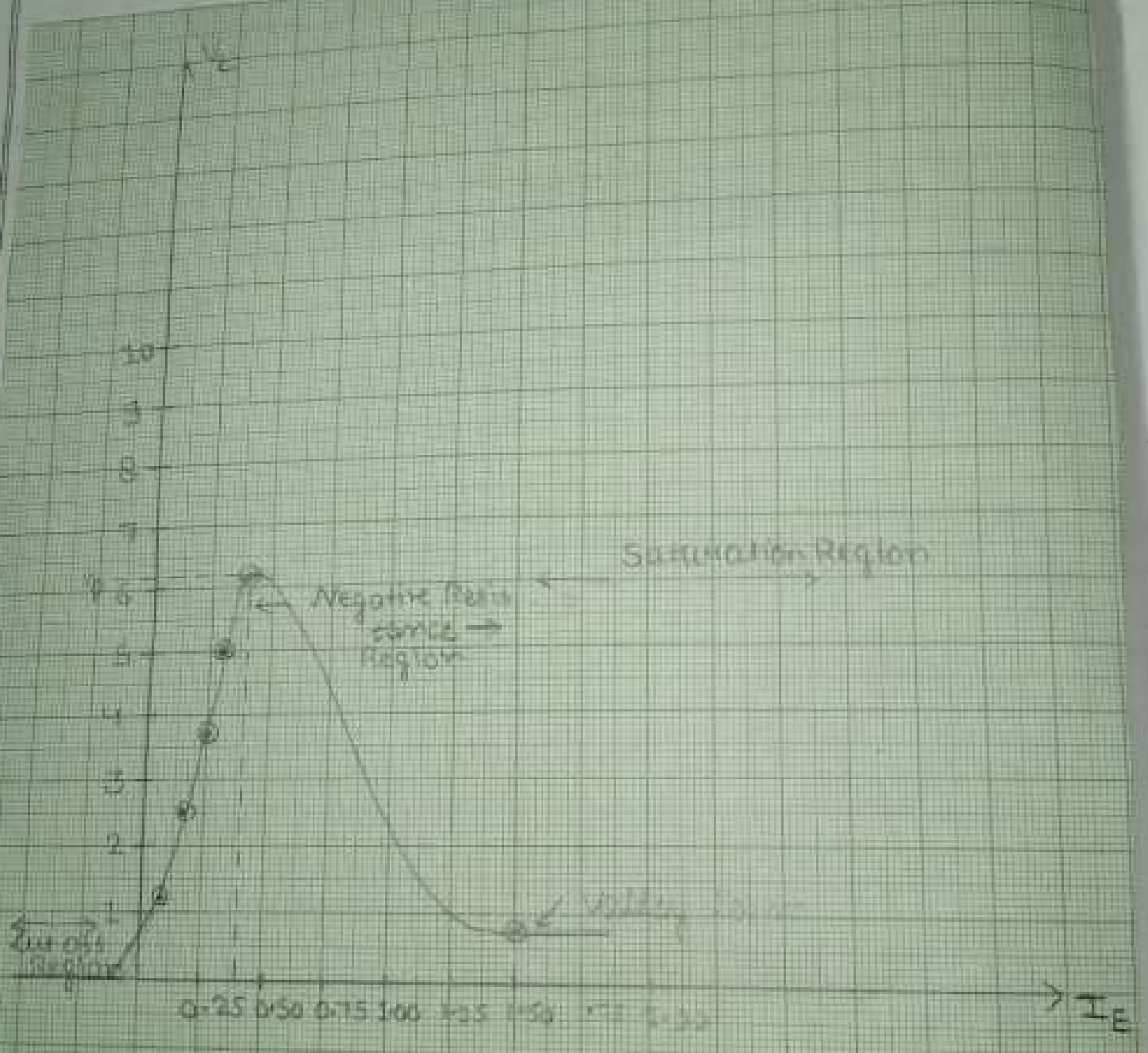

Expt. No. _____

VJT Characteristics

S. NO	V (Volts)	I (mA)
1	1.25	0.075
2	2.5	0.15
3	3.75	0.25
4	5	0.325
5	6.25	0.4
6	0.75	1.5

• Result - The characteristics of VJT have been plotted.

• Precaution -

- (1) Always connect the voltmeter in parallel & ammeter in series as shown in fig.
- (2) connection should be proper & tight.
- (3) Switch 'ON' the supply after completing the CRT.
- (4) DC supply should be increased slowly in steps.
- (5) Reading of voltmeter & ammeter should be accurate.

Teacher's Signature _____